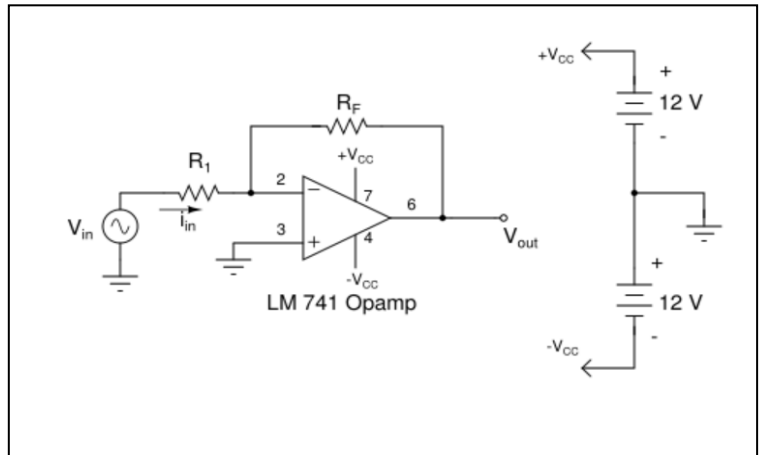


Pre-lab Quiz for EE Expt 2 / Sample Set

Duration: 10 min. Marks: 5×1 mark = 5 marks. No partial marks for any of the questions. Do your rough work in this paper itself. No extra sheets will be given. No clarifications/explanations will be given.

- 1) The inverting amplifier circuit of Expt 2 is shown in the figure, Given: $v_{in}(t) = 0.5 \sin(\omega t + \theta)$ V of frequency 1 kHz, $R_1 = 4 \text{ k}\Omega$, $R_F = 1 \text{ k}\Omega$. Mark **all the correct options** with regard to this circuit.



- A) The voltage gain is -4 .
- B) The voltage gain is -0.25 .
- C) V_{in} is a differential signal, and V_{out} is a single-ended signal.
- D) V_{in} is a single-ended signal, and V_{out} is also a single-ended signal.
- E) The input resistance (V_{in}/I_{in}) is $4 \text{ k}\Omega$.
- F) The input resistance (V_{in}/I_{in}) is $1 \text{ k}\Omega$.
- G) The circuit qualifies as an amplifier because it can provide a power gain larger than unity.
- H) The circuit qualifies as an amplifier because the output voltage amplitude is larger than the input voltage amplitude.

Answer(s): _____

- 2) In the circuit shown above, $R_1 = 2 \text{ k}\Omega$, $R_F = 20 \text{ k}\Omega$. Assume that the v_{out} limits are $+V_{cc}$ and $-V_{cc}$. Mark **all the correct options** with regard to this circuit.
- A) The input $v_{in}(t)$ is a triangular wave going from -2 V to $+2 \text{ V}$. The output $v_{out}(t)$ will also be a triangular wave.
 - B) The input $v_{in}(t)$ is a square wave with the maximum and minimum levels of $+2 \text{ V}$ and -2 V . The output $v_{out}(t)$ will be a square wave with the maximum and minimum levels of $+20 \text{ V}$ and -20 V .
 - C) The input $v_{in}(t)$ is a square wave with the maximum and minimum levels of $+2 \text{ V}$ and -2 V . The output $v_{out}(t)$ will be a square wave with the maximum and minimum levels $+12 \text{ V}$ and -12 V .
 - D) If the connections to the op amp input terminals are interchanged, the circuit will not work as a linear amplifier.
 - E) If the connections to the op amp input terminals are interchanged, the circuit will work as a non-inverting amplifier.


Answer(s): _____

3&4) The current-to-voltage converter circuit of Expt 2 is shown in the figure. Given: $R_1 = 10\text{ k}\Omega$, $R_F = 20\text{ k}\Omega$, $+V_{cc} = +12\text{ V}$, $-V_{cc} = -12\text{ V}$.

A rectifier diode is connected as the device-under-test (DUT) with its cathode at terminal B and anode at terminal C. The diode I-V characteristic has a forward voltage drop of 0.6 V , and negligible reverse saturation current. Calculate the current through the device (I_{DUT}) and the voltage across it (V_{DUT}) at the instant when $V_{AFG} = +5.6\text{ V}$.

$I_{DUT} = \underline{\hspace{2cm}}\text{ mA}$

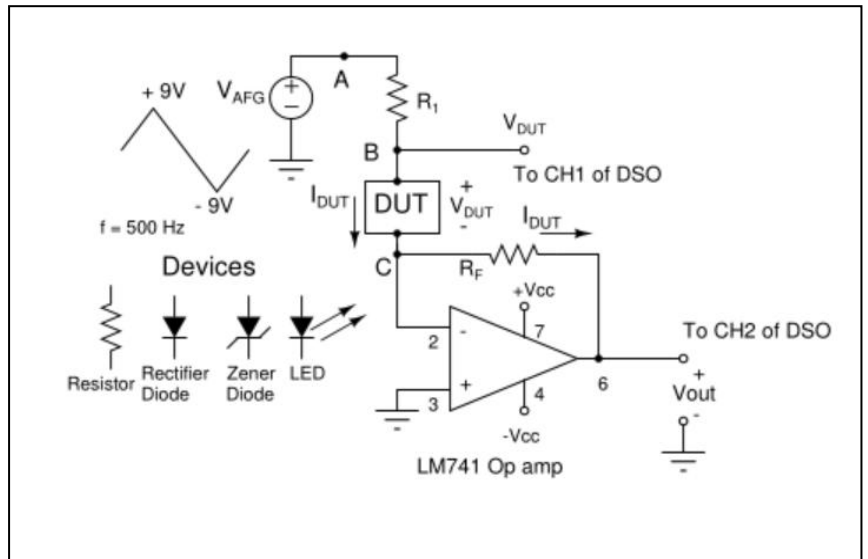$V_{DUT} = \underline{\hspace{2cm}}\text{ V}$



- 5) In the circuit shown above, $R_1 = 10\text{ k}\Omega$, $R_F = 20\text{ k}\Omega$, $+V_{cc} = +12\text{ V}$, $-V_{cc} = -12\text{ V}$. A resistor of $2\text{ k}\Omega$ is connected across the nodes B and C as the device-under-test (DUT). Calculate output voltage (V_{out}) at the instant when $V_{AFG} = -3\text{ V}$.

$V_{out} = \underline{\hspace{2cm}}\text{ V}$
