

Name:

Roll No.

Signature :

Room No.:

Feb 27, 2025 (Thu)

MS101 – Makerspace 2024-25/II (Spring Semester)**EE Mid-semester Examination****Time: 2 hours****Marks: 50**

1. This **Question-cum-Answer Booklet** has 8 pages and 20 questions.
2. Write your **answers only in the space provided for answers**. Answers written at any other place will not be checked. You may use the page margins also for rough work.
3. No explanations / clarifications will be given to any of the questions.
4. No negative marks for wrong answers, **however, steps are required for all numerical answers.**
5. **In case of questions with multiple-choices, credit will be given only if all correct options are identified.**

Q.no.	1	2	3	4	5	6	7	8	9	10	11	12
Marks												
Q.no.	13	14	15	16	17	18	19	20			TOTAL	
Marks												

1. An RC low-pass filter is designed with a resistor R and a capacitor C for use with an input signal containing multiple frequency components. Write all the correct options out of the following statements regarding the filter's behaviour.
 - A) Frequencies much lower than the cut-off frequency (f_c) pass through the filter to the output with minimal attenuation.
 - B) Frequencies much higher than the cut-off frequency (f_c) pass through the filter to the output with minimal attenuation.
 - C) Frequencies much higher than the cut-off frequency (f_c) are significantly attenuated.
 - D) Frequencies much lower than the cut-off frequency (f_c) are significantly attenuated.
 - E) At the cut-off frequency (f_c), amplitude of the output voltage is reduced to approximately 70.7% of the input voltage.

Answer(s):

Mark: 1

2. Write all the correct options out of the following statements for an N-channel enhancement mode MOSFET.
 - A) The channel exists only when a gate voltage less than the threshold voltage is applied.
 - B) The channel exists only when a gate voltage greater than or equal to the threshold voltage is applied.
 - C) Holes form the conduction channel.
 - D) Electrons form the conduction channel.
 - E) The threshold voltage is negative.
 - F) The threshold voltage is positive.

Answer(s):

Mark: 1

Rough work

3. A practical voltage source is modelled as an ideal voltage source of 15 V in series with a source resistance R_S . When a load resistance was connected across this source, the current drawn from the source was 400 mA and its terminal voltage V_{Term} dropped to 13 V.
- A) Evaluate R_S in ohms.
- B) If a $400\ \Omega$ resistance is connected across the voltage source what will be V_{Term} in V?
- No marks without steps.*

Marks: 2[=1+1]


A) $R_S = \dots\dots\dots \Omega$

B) $V_{\text{Term}} = \dots\dots\dots \text{ V}$

4. A resistive network is given below. $V_A = 12\text{ V}$, $V_B = 9\text{ V}$, $R_A = R_B = R_L = 300\ \Omega$. Evaluate the node voltage V_X and current I_L . Hint: Use superposition method.
- No marks without steps.*

Marks: 3[=1.5 +1.5]

Steps:

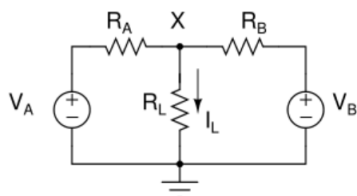


$V_X = \dots\dots\dots \text{ V} ; \quad I_L = \dots\dots\dots \text{ mA}$

5. An RC filter circuit is shown below. $R = 2.5\text{ k}\Omega$. Its cut-off frequency f_c was found to be 1570 Hz. Its gain A is given by:

$$A = \left| \frac{V_{\text{out}}}{V_{\text{in}}} \right| = \frac{1}{[1+(\omega CR)^2]^{1/2}} = \frac{1}{[1+(f/f_c)^2]^{1/2}}$$

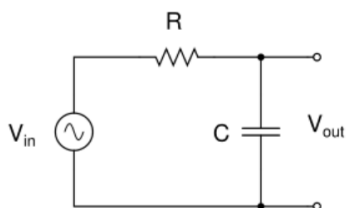where $\omega = 2\pi f$ and $f_c = 1/(2\pi RC)$.



- A) Evaluate C in μF .
- B) Evaluate the magnitude of A at $f = 0$ and at $f = f_c$.
(No partial credit for this part; 1 mark only if both answers are correct).

Marks: 2[=1+1]


Answers:


A) $C = \dots\dots\dots \mu\text{F}$.

B) Magnitude of A at $f = 0$: $\dots\dots\dots$

Magnitude of A at $f = f_c$: $\dots\dots\dots$

Rough work:

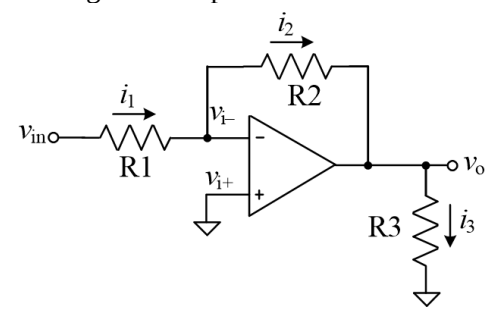6. In the op-amp circuit shown in the figure, $R_1 = 40\text{ k}\Omega$, $R_2 = 10\text{ k}\Omega$, $R_3 = 1000\text{ }\Omega$. Find the voltage, current, and power gains. Is it serving as an amplifier? 	Marks: 4 [= 1 x 4] A) Voltage gain $A_v = v_o / v_{in}$ Steps: Answer:..... B) Current gain $A_i = i_3 / i_1$ Steps: Answer:..... C) Power gain $A_p = A_v A_i$ Steps: Answer:..... D) Is it serving as an amplifier? Write Yes or No. Answer:.....
--	---

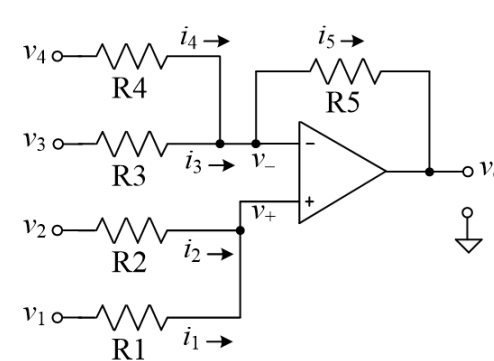7. In the summer circuit shown in the figure, $R_1 = R_2 = R_3 = 10\text{ k}\Omega$, $R_4 = R_5 = 80\text{ k}\Omega$. Find the voltage gain and input resistance for the second and third inputs. 	Marks: 4 [-2+0.5+1+0.5] A) $A_{v1} = v_o / v_1$ Steps: Answer:..... B) $R_{in1} = v_1 / i_1$ Answer:..... C) $A_{v4} = v_o / v_4$ Steps: Answer:..... D) $R_{in4} = v_4 / i_4$ Answer:.....
---	--

Q7 dropped.

8. Convert the decimal number 251 to its binary format. Mark: 1 Binary format:

9. Convert the decimal number 190 to its hexadecimal format. Mark: 1 Hexadecimal format:

Rough work:

10. Convert the binary number 11001101 to its decimal format.


Mark: 1

Decimal format:

11. A digital circuit is shown below.

A) Write the truth table for **Out**.

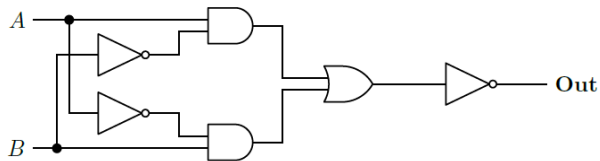B) Write the Boolean expression for **Out**.



Marks: 2[=1+1]

A) Truth table

A	B	Out
0	0	
0	1	
1	0	
1	1	

B) **Out** =

12. Consider the 2's complement representation which occupies a total of 5 bits, including the sign bit.

Marks: 4[=2+1+1]

A) Obtain the 2's complement representation of -12.

Steps:

Answer:

B) Give the 2's complement representation of 3.

Answer:

C) Obtain the 2's complement representation of 3-12.

Steps:

Answer:

13. A battery operated DC motor runs on 10 V and its coil resistance is 100 Ω .

A) Calculate the current consumed by the motor at the start (no 'back emf').

B) The motor is rotating and it takes 20 mA of current. Calculate the 'back emf' offered by the motor coil.

Marks: 2[=1+1]

Steps:

A) Current at start = mA

B) Back emf = V

=====

Rough work:

14. The truth table for a digital circuit with output **F_n** and inputs *A*, *B*, *C*, and *D* (with *A* as the most significant bit) is shown below.

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	F_n
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

- A) Express **F_n** in canonical form as a sum of products.
 B) Fill entries in the Karnaugh map shown for **F_n** as a function of *A*, *B*, *C*, and *D*. Show the maximal groupings of 1's in the Karnaugh map and derive the minimal logic expression for **F_n** in terms of *A*, *B*, *C*, *D* and their complements.

Marks: 6[=3+3]

A) **F_n** =

B) K-map and minimized **F_n**

<i>AB</i> ↓ <i>CD</i> →	00	01	11	10
00				
01				
11				
10				


F_n =

=====

Rough work:

15. Op amp based current-to-voltage converter circuit of Expt 2 is shown below. Given: $R_1 = 2\text{ k}\Omega$, $R_F = 3\text{ k}\Omega$, $+V_{CC} = +12\text{ V}$, $-V_{CC} = -12\text{ V}$. A Zener diode is connected as the device-under-test (DUT) with its anode at terminal B and cathode at terminal C. The Zener voltage is 6.5 V . Calculate the current through the Zener diode (I_{DUT}), V_{DUT} and V_{out} at the instant when $V_{AFG} = -9\text{ V}$.

Marks: 4[=1.5+1.5+1]

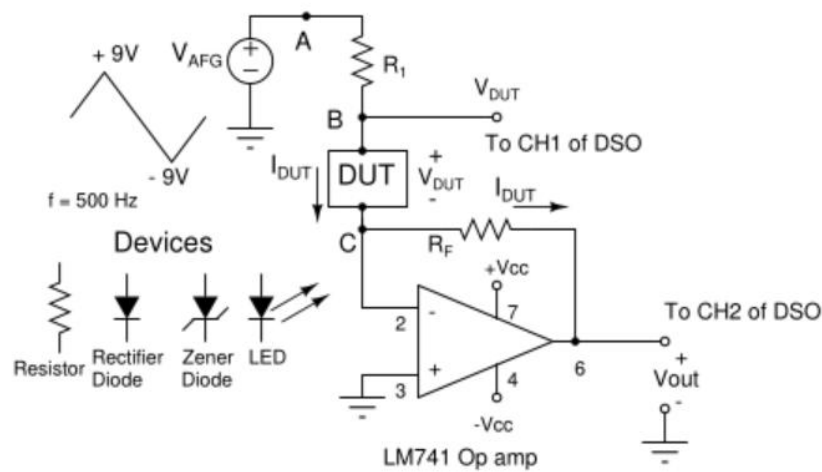

Show steps:

$I_{DUT} = \dots\dots\dots \text{ mA.}$

$V_{DUT} = \dots\dots\dots \text{ V.}$

$V_{out} = \dots\dots\dots \text{ V.}$


16. In an attracted armature relay, the coil proportionality constant is $K = 2.4\text{ N.A}^{-2}$. And the restraining force (C) of the coil is 0.184 N . Find the current through the coil so that the force on the armature is 0.2 N . (Force equation: $F = K \times I^2 - C$)

Steps:

Mark: 1

Current through coil = $\dots\dots\dots \text{ A}$

Rough work:

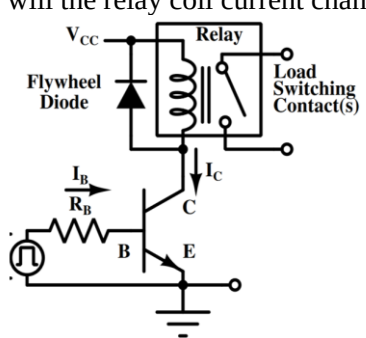
17. A relay circuit is shown below where an input control pulse of 10 V is applied to base resistor (R_B). The relay coil activation current is 80 mA and $R_B = 4.6 \text{ k}\Omega$. Assume $V_{BEsat} = 0.8 \text{ V}$ and $V_{CEsat} = 0.2 \text{ V}$ and $V_{CC} = 10 \text{ V}$. A) What should be the minimum value of β (i.e. β_{min}) for the relay to operate? B) If the relay coil resistance is 100Ω, and the BJT has $\beta = 50$, what will be the current through the relay? C) If the load connected across the 'load switching contacts' of the relay is changed to half the current, will the relay coil current change? 	Marks: 4[=1+2+1] A) β_{min} Steps: $\beta_{min} = \dots\dots\dots$ B) Current through the relay in mA: Steps: Current through the relay = $\dots\dots\dots \text{ mA}$ C) Answer: choose the correct option from below. i) will increase ii) will decrease iii) will remain the same $\dots\dots\dots$
---	---

18. Which of the following interfaces does the Arduino Nano board support? Write all the correct options. A) 4 Analog inputs. B) 10 Digital I/Os. C) 14 Digital I/Os. D) 8 Analog inputs. E) An SPI bus interface. F) A UART interface. Answer(s): $\dots\dots\dots$ Mark: 1
--

19. "Using the Arduino board for a motor control application, it is possible to implement a digital-to-analog converter". Write all the correct options with regard to this statement. A) True, but the Arduino board will need additional circuitry. B) False, it is impossible to implement a digital-to-analog converter using the Arduino board. C) True, it is possible to do so using only software, without additional circuitry. D) True, using only software, i.e. without additional circuitry, the resolution can be better than 5% of the 5 V reference voltage. E) True, using only software, i.e. without additional circuitry, the resolution can be better than 0.1% of the 5 V reference voltage. F) True, Arduino board has an inbuilt hardware digital-to-analog converter. Answer(s): $\dots\dots\dots$ Mark: 1

Rough work:

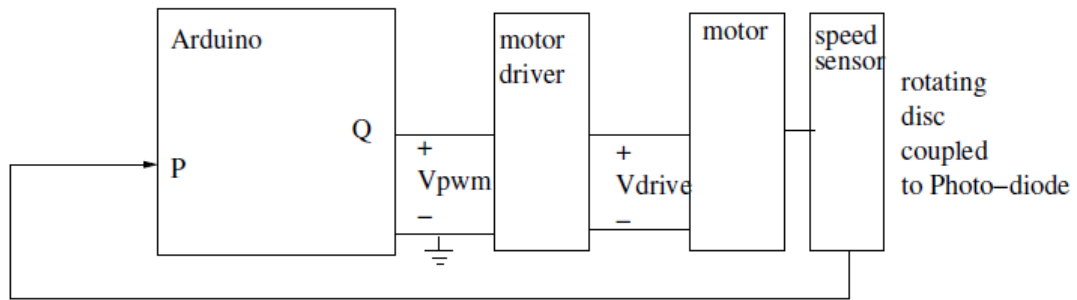20. Consider the system setup shown below which is the same speed measurement setup you used in Expt 4 with the BO motor. The BO motor is loaded with a torque T .



For the fixed load torque T and average of the applied voltage V_{PWM} , assume that the equation for the motor speed is given by: $\text{Speed (RPM)} = (k_1 V_{PWM}) - k_2$, where k_1 and k_2 are BO constants.

Assume that you are given all the instruments and accessories used in Expt 4 (i.e. DSO, Keithley Power Supply, L298 Motor driver card, Arduino Nano board, and the Arduino sketch used in Expt 4, the sensor PCB, rotating disc, etc).

A) Using all the Expt 4 setup how will you measure the speed of the motor in RPM? Give your answer in just three to four steps. Give a valid PWM value and give your measurement steps.

Step1:

Step 2:

Step 3:

Step 4:

B) How will you estimate k_1 ? (Give your answer in just two sentences)

.....

C) How will you estimate k_2 ? (Give your answer in just two sentences)

.....

Marks: 5[=3+1+1]

Rough work: