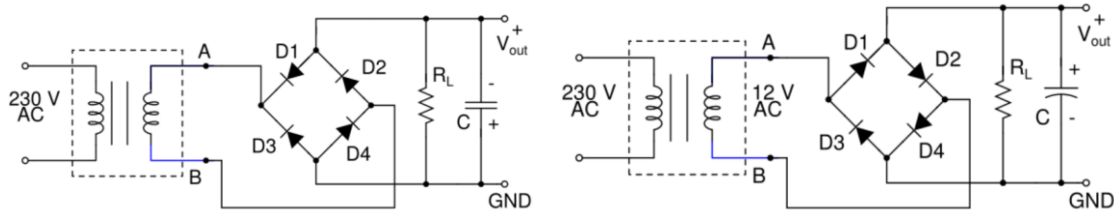



Sample Problems

- Two wrong bridge rectifier circuits with a capacitor filter are given below. Rectify the mistakes and draw them correctly.




- The half-wave rectifier circuit shown below, uses a 230 V(RMS) to 12 V(RMS) step-down transformer.

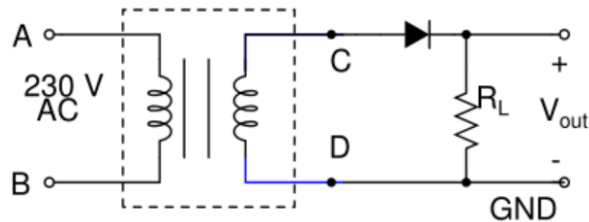- If resistor R_L is removed from the circuit, what will be V_{out} in volts?
- If the diode is now reversed, sketch V_{out} .



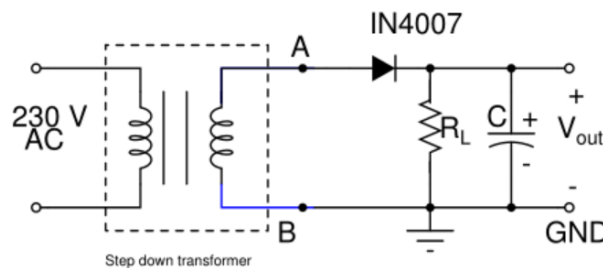- The rectifier circuit shown below uses a 230 V (RMS) to 15 V (RMS) step-down transformer.



- Evaluate the average value of V_{out} if C is removed.
- With the capacitor C present and the load resistor R_L not present or very large, evaluate V_{out} .
- Find the V_{out} as in (B) if the transformer input voltage is 115 V (RMS).

4. Which of the following unregulated DC power supplies, all having the same output DC voltage (average value of V_{out}), has the highest peak-to-peak ripple voltage?
- A) An unregulated DC power supply made of a half-wave rectifier with load resistance $R_L = 2 \text{ k}\Omega$ and a filter capacitance $C = 100 \text{ }\mu\text{F}$.
- B) An unregulated DC power supply made of a half-wave rectifier with load resistance $R_L = 2 \text{ k}\Omega$ and a filter capacitance $C = 1000 \text{ }\mu\text{F}$.
- C) An unregulated DC power supply made of a bridge rectifier with load resistance $R_L = 2 \text{ k}\Omega$ and a filter capacitance $C = 100 \text{ }\mu\text{F}$.
- D) An unregulated DC power supply made of a bridge rectifier with load resistance $R_L = 2 \text{ k}\Omega$ and a filter capacitance $C = 1000 \text{ }\mu\text{F}$.

5. Two rectifier circuits are shown below. With reference to these circuits **mark all statements that are correct**.

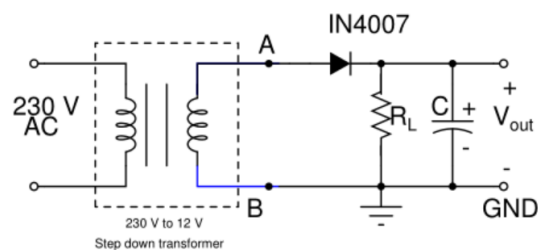


Fig 5A

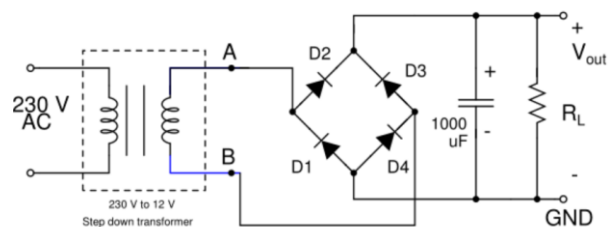


Fig 5B

- A) For the same values of R_L and C , the average value of V_{out} of the circuit in Fig 5A will be greater than that in Fig. 5B.
- B) For the same values of R_L and C , the average value of V_{out} of the circuit in Fig 5B will be less than that in Fig. 5A.
- C) For the same values of R_L and C , the average values of V_{out} of the circuits in Fig 5A and Fig 5B will be the same.
- D) For the same values of R_L and C , the peak-to-peak ripple voltage in V_{out} of the circuit in Fig 5A will be greater than that in Fig 5B.
- E) For the same values of R_L and C , the peak-to-peak ripple voltage in V_{out} of the circuit in Fig 5B will be greater than that in Fig 5A.
- F) For the same values of R_L and C , the peak-to-peak ripple voltages in V_{out} of the circuits in Fig 5A and Fig 5B will be the same.
6. The circuit diagram for a clipping circuit for peak limiting is shown below in Fig P6. Given: $R = 2 \text{ k}\Omega$, diode forward voltage drop $= 0.7 \text{ V}$, $v_i = 6 \sin \omega t$.
- A) What is the maximum value of the diode current in mA?
- B) What are the minimum and maximum values of v_o in volts?
- C) Sketch v_i and superimpose on it the diode current and the v_o waveform.

7. The circuit diagram for a clipping circuit for valley limiting is shown below in Fig P7. Given: $R = 2 \text{ k}\Omega$, diode forward voltage drop $= 0.7 \text{ V}$, $v_i = 6 \sin \omega t$.

- What is the maximum value of the diode current in mA?
- What are the minimum and maximum values of v_o in volts?
- Sketch v_i and superimpose on it the diode current and the v_o waveform.

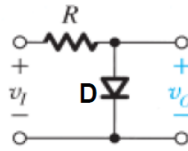


Fig P6

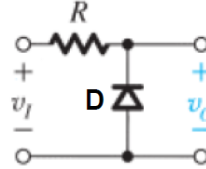


Fig P7

8. The circuit diagram for a clipping circuit for peak and valley limiting is shown below in Fig P8. Given: $R = 2 \text{ k}\Omega$, diode forward voltage drop $= 0.7 \text{ V}$, $v_i = 6 \sin \omega t$.

- What are the minimum and maximum values of the diode current in mA?
- What are the minimum and maximum values of v_o in volts?
- Sketch v_i and superimpose on it the two diode currents and the v_o waveform.


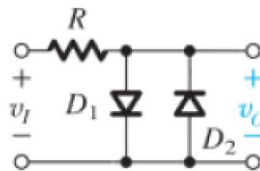



Fig P8

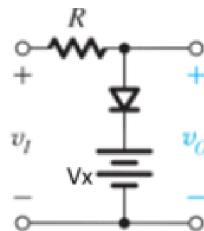9. The circuit diagram for a clipping circuit for peak limiting with a voltage source is shown below in Fig P9. Given: $R = 2 \text{ k}\Omega$, $V_x = 2 \text{ V}$, diode forward voltage drop $= 0.7 \text{ V}$, $v_i = 6 \sin \omega t$.




- What is the maximum value of the diode current in mA?
- What are the minimum and maximum values of v_o in volts?
- Sketch v_i and superimpose on it the diode current and the v_o waveform.

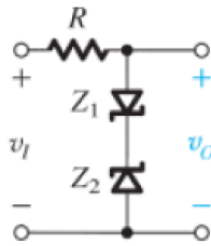10. The circuit diagram for a clipping circuit using Zener diodes is shown below in Fig P10. Given: $R = 2 \text{ k}\Omega$, $V_{Z1} = V_{Z2} = 3 \text{ V}$, $v_i = 8 \sin \omega t$. Assume that the Zener diodes have forward voltage drop of 0.7 V and vertical I-V characteristic in the breakdown region.



- A) What are the minimum and maximum values of the current through the Zener diodes in mA?
- B) What are minimum and maximum values of v_O in volts?
- C) Sketch v_I and superimpose on it the diode current and the v_O waveform.

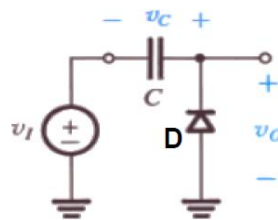11. A clamping circuit is shown in Fig P11. Given: $v_I = 4 + 8 \sin \omega t$ V, diode D is ideal, i.e. it has zero forward voltage drop.



- A) In the steady state, i.e. several cycles of v_I , what will be the value of v_C in volts?
- B) What will be the peak value of v_O in volts?
- C) What will be the minimum voltage of v_O in volts?
- D) Sketch v_I and superimpose on it the v_O waveform.
